

Министерство образования Республики Беларусь  
Учреждение образования «Белорусский государственный университет  
информатики и радиоэлектроники»

Факультет компьютерных систем и сетей

Кафедра электронных вычислительных средств

Дисциплина: Проектирование цифровых систем на языках описания аппаратуры

ОТЧЕТ  
к лабораторной работе №4  
на тему

ОПИСАНИЕ И МОДЕЛИРОВАНИЕ ТРИГГЕРОВ И КОНЕЧНЫХ АВТОМАТОВ

Выполнили:  
ст. гр. 850702  
Турко В. Д.

Проверил:  
Санько Н. С.

Минск 2020

# 1 МОДЕЛИРОВАНИЕ ТРИГГЕРА

## 1.1 Цель работы

С использованием девятизначного алфавита STD\_LOGIC составить VHDL-модель и провести моделирование триггера двумя способами: по логической схеме и по таблице функционирования триггера.

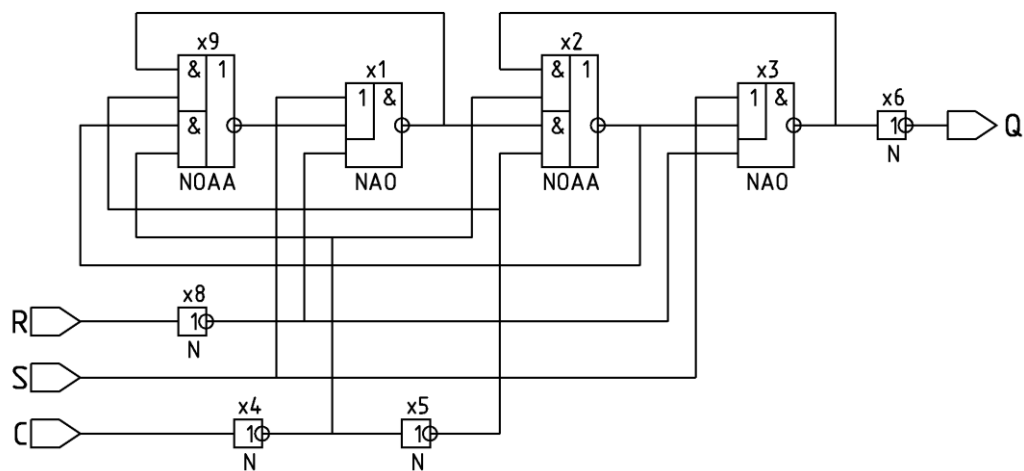


Рисунок 1.1 – Логическая схема

**Таблица истинности**

R	S	C	Q
1	-	[--]	0
0	1	[--]	1
0	0	[01]	$\neg(Q)$
0	0	[1-]	N
0	0	[00]	N

Рисунок 1.2 – Таблица истинности

## 1.2 vhdl-модель триггера

В таблице 2.1 приведена реализация моделей триггера согласно заданию.

Таблица 2.1 – модели элементов

<pre>LIBRARY ieee; USE ieee.std_logic_1164.ALL; USE work.lib_package.ALL;  ENTITY TriggerScheme IS   PORT (     R, S, C : IN STD_LOGIC;</pre>	<pre>LIBRARY ieee; USE ieee.std_logic_1164.ALL;  ENTITY TriggerAlgorithm IS   PORT (     R, S, C : IN STD_LOGIC;     Q : INOUT STD_LOGIC);</pre>
---	--

<pre>         Q : INOUT STD_LOGIC); END TriggerScheme; ARCHITECTURE SchemeArch OF TriggerScheme IS      SIGNAL x : STD_LOGIC_VECTOR(9 DOWNT0 1);  BEGIN     X9 : NOAA PORT MAP(x(1), x(5), x(2), x(4), x(9));     X8 : N PORT MAP(R, x(8));     X6 : N PORT MAP(x(3), Q);     X5 : N PORT MAP(x(4), x(5));     X4 : N PORT MAP(C, x(4));     X3 : NAO PORT MAP(S, x(2), x(8), x(3));     X2 : NOAA PORT MAP(x(3), x(4), x(1), x(5), x(2));     X1 : NAO PORT MAP(S, x(9), x(8), x(1)); END ARCHITECTURE SchemeArch; </pre>	<pre> END TriggerAlgorithm;  ARCHITECTURE AlgorithmArch OF TriggerAlgorithm IS     FUNCTION rising_edge (SIGNAL s : STD_LOGIC)         RETURN BOOLEAN IS     BEGIN         RETURN s = '1' AND s'event;     END;  BEGIN     PROCESS(R, S, C)     BEGIN         IF R = '1' THEN             Q &lt;= '0' after 8 ns;         ELSIF S = '1' THEN             Q &lt;= '1' after 8 ns;         ELSE             IF rising_edge(C) THEN                 Q &lt;= NOT Q after 13 ns;             ELSE                 Q &lt;= Q after 2 ns;             END IF;         END IF;     END PROCESS; END ARCHITECTURE AlgorithmArch; </pre>
--	--

### 1.3 Моделирование триггера

Тестирующая программа:

```

ENTITY TEST_BENCH IS
END TEST_BENCH;

ARCHITECTURE MainBehavior OF TEST_BENCH IS

    COMPONENT TriggerScheme IS
        PORT (
            R, S, C : IN STD_LOGIC;
            Q : INOUT STD_LOGIC);
    END COMPONENT TriggerScheme;

    COMPONENT TriggerAlgorithm IS
        PORT (
            R, S, C : IN STD_LOGIC;
            Q : INOUT STD_LOGIC);
    END COMPONENT TriggerAlgorithm;

```

```

    SIGNAL r_test : STD_LOGIC;
    SIGNAL S_test : STD_LOGIC;
    SIGNAL c_test : STD_LOGIC;
    SIGNAL q_scheme : STD_LOGIC;
    SIGNAL q_alg : STD_LOGIC;

BEGIN

    p1 : TriggerScheme PORT MAP(r_test, S_test, c_test, q_scheme);
    p2 : TriggerAlgorithm PORT MAP(r_test, S_test, c_test, q_alg);

    PROCESS IS
    BEGIN
        r_test <= '1';
        WAIT FOR interval * 2;
        r_test <= '0';
        WAIT;
    END PROCESS;

    PROCESS IS
    BEGIN
        S_test <= '0';
        WAIT FOR interval;
        S_test <= '1';
        WAIT FOR interval * 4;
        S_test <= '0';
        WAIT;
    END PROCESS;

    PROCESS IS
    BEGIN
        c_test <= '0';
        WAIT FOR interval;
        c_test <= '1';
        WAIT FOR interval;
    END PROCESS;

    PROCESS IS
        VARIABLE count : INTEGER := 8;
    BEGIN
        IF count < 1 THEN
            stop;
        ELSE
            count := count - 1;
            WAIT FOR interval;
        END IF;
    END PROCESS;

END MainBehavior;

```

В результате моделирования получим временную диаграмму, представленную на рис. 2.1.

 


Рисунок 2.1 – Временная диаграмма

## 2 МОДЕЛИРОВАНИЕ АВТОМАТА МИЛИ

### 2.1 Цель работы

Составить VHDL-описание конечного автомата Мили, заданного совмещенной таблицей переходов (таблица 2.1).

Таблица 2.1 – модели элементов

Входные сигналы	Состояния			
	a1	a2	a3	a4
Z1	a3/w5	a2/w1	a2/w2	a11/w5
Z2	a4/w5	a2/w5	a4/w3	a3/w3
Z3	a3/w5	a1/w4	a1/w4	a11/w5

### 2.2 VHDL-модель автомата Мили

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY Mealy IS
  PORT (
    clk, rst : IN STD_LOGIC;
    x : IN STD_LOGIC_VECTOR(1 TO 2);
    y : OUT STD_LOGIC_VECTOR(1 TO 3));
END Mealy;

ARCHITECTURE rtl OF Mealy IS

  TYPE T_state IS (a1, a2, a3, a4);
  SIGNAL state : T_state := a1;
  SIGNAL NEXT_state : T_state;

```

BEGIN

```
manageCase : PROCESS (state, x)
BEGIN
  IF ((x(1) AND x(2)) = '0') THEN
    CASE state IS
      WHEN a1 =>
        IF (x(2) = '0') THEN -- '00' || '10'
          NEXT_state <= a3;
        ELSE
          NEXT_state <= a4;
        END IF;
        y <= "000";
      WHEN a2 =>
        CASE x IS
          WHEN "00" => NEXT_state <= a2; y <= "100";
          WHEN "01" => NEXT_state <= a2; y <= "000";
          WHEN "10" => NEXT_state <= a1; y <= "001";
          WHEN OTHERS => NEXT_state <= state;
        END CASE;
      WHEN a3 =>
        CASE x IS
          WHEN "00" => NEXT_state <= a2; y <= "011";
          WHEN "01" => NEXT_state <= a4; y <= "010";
          WHEN "10" => NEXT_state <= a1; y <= "001";
          WHEN OTHERS => NEXT_state <= state;
        END CASE;
      WHEN a4 =>
        IF (x(2) = '0') THEN -- '00' || '10'
          NEXT_state <= a1; y <= "000";
        ELSE
          NEXT_state <= a4; y <= "010";
        END IF;
      END CASE;
    END IF;
  END PROCESS manageCase;
  state <= a1 WHEN rst = '1' ELSE
    NEXT_state WHEN clk'event AND clk = '1' ELSE
    state;
END rtl;
```

## 2.3 Моделирование

Тестирующая программа:

```
ENTITY SCHEME_TEST IS
END SCHEME_TEST;
```

```

ARCHITECTURE MainBehavior OF SCHEME_TEST IS
  COMPONENT Mealy IS
    PORT (
      clk, rst : IN STD_LOGIC;
      X : IN STD_LOGIC_VECTOR(1 TO 2);
      y : OUT STD_LOGIC_VECTOR(1 TO 3));
  END COMPONENT Mealy;

  SIGNAL clk : STD_LOGIC;
  SIGNAL rst : STD_LOGIC := '1';
  SIGNAL X : STD_LOGIC_VECTOR(1 TO 2) := (OTHERS => '0');
  SIGNAL y : STD_LOGIC_VECTOR(1 TO 3);


  CONSTANT clk_period : TIME := 20 ns;
BEGIN
  p1 : Mealy PORT MAP(clk, rst, x, y);

  clk_process : PROCESS
  BEGIN
    clk <= '1'; WAIT FOR clk_period/2;
    clk <= '0'; WAIT FOR clk_period/2;
  END PROCESS;

  rst_process : PROCESS
  BEGIN
    WAIT FOR clk_period;
    rst <= '0';
    WAIT;
  END PROCESS;


  PROCESS IS
    VARIABLE count : INTEGER := 8;
    VARIABLE tmp : STD_LOGIC_VECTOR(3 DOWNT0 0) := (OTHERS => '0');
  BEGIN
    IF count < 0 THEN
      stop;
    ELSE
      tmp := STD_LOGIC_VECTOR(to_unsigned(count, 4));
      x <= tmp(1 DOWNT0 0); WAIT FOR 50 ns;
      count := count - 1;
    END IF;
  END PROCESS;
END MainBehavior;

```

 

Скрипт:
 
```
*x0 соответствует x(1), x1 – x(2)
vsim -novopt mealy
force clk '1' 0, '0' 10 -repeat 20
force rst '1' 0, '0' 20 -repeat 180
force x0 '0' 0, '1' 20, '1' 40, '0' 60 -repeat 80
force x1 '0' 0, '1' 20, '0' 40, '1' 60 -repeat 80
add wave *
view wave
run 180 ns
quit –sim
```



### 3 ВЫВОД

При выполнении лабораторной работы я составил структурное и алгоритмическое VHDL-описания для двухтактного Т-триггера со сбросом и установкой и провел моделирование данных описаний, которые дали идентичный результат.

Также составил VHDL-модель конечного автомата Мили и провел моделирование с помощью тестирующей программы и скрипта, получив одинаковые результаты.